

Series and Parallel Circuits

Electrical Engineering

Wolfgang Neff

Series and Parallel Circuits (1)

- Electrons are easy-going guys




Series and Parallel Circuits (2)

- Series means there is no option




Series and Parallel Circuits (3)

- Parallel means there is an option

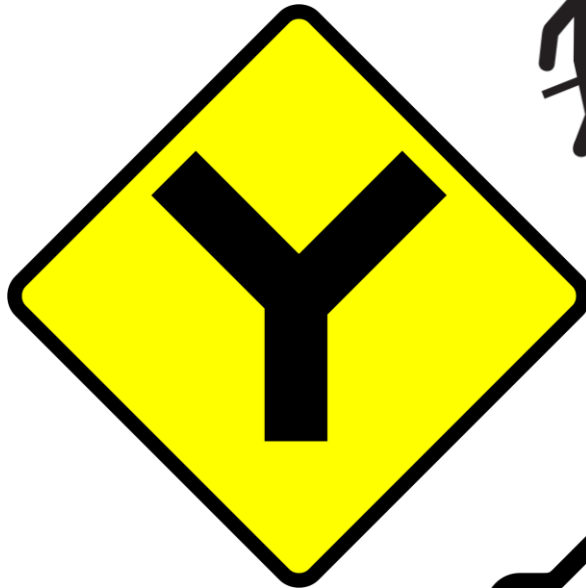

Series and Parallel Circuits (4)


- Series – a schematic view

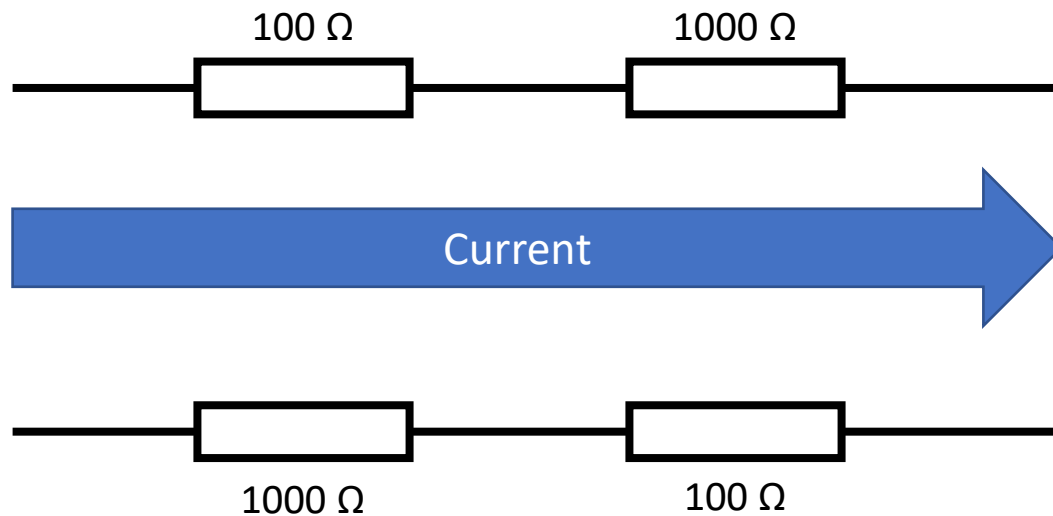

In any case, the current must go through

Series and Parallel Circuits (5)

- Parallel – a schematic view

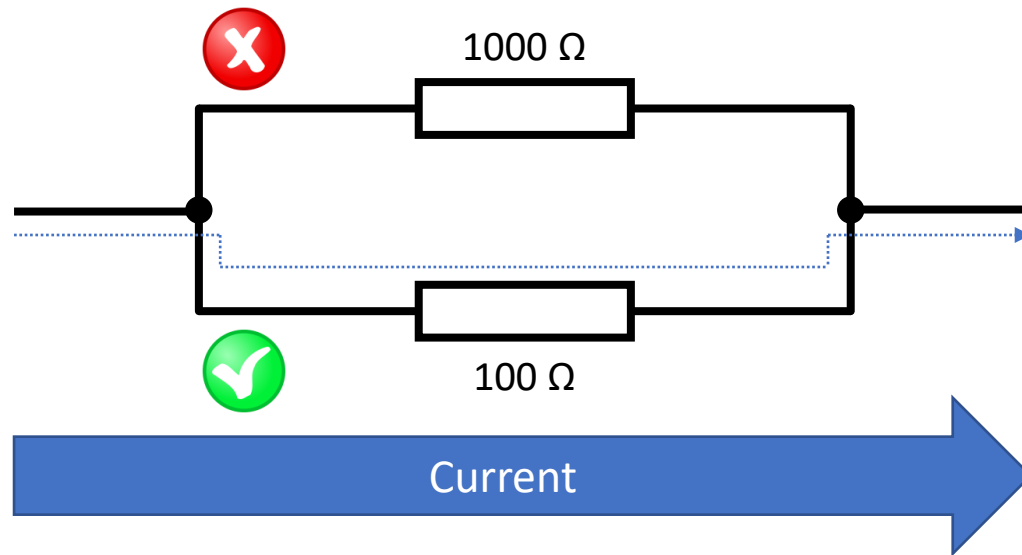

There is an easy way to go