


Prescalers

Digital Electronics

by Wolfgang Neff

Prescalers (1)

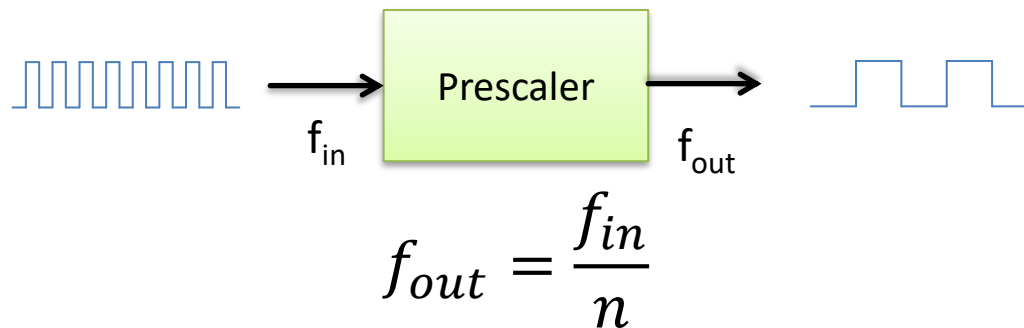- Reduces the frequency of an input signal
 - Also called
 - Clock divider
 - Frequency divider
 - Divides the input frequency by a factor



Prescalers (2)

- Frequency is Reduced by Counting

– Example


- Mod-8 counter \rightarrow 3 binary digits (Q_0, Q_1, Q_2)

| Ticks | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | Div | | |
|-------|---|---|---|---|---|---|---|---|-----|---|---|
| Clock | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| Q_0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 2 |
| Q_1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 4 |
| Q_2 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 8 |

Prescalers (3)

- Implementation


- Use T flip-flops (toggles its state)

 

| Q ⁺ | Action |
|----------------|--------------|
| -Q | Toggle state |


- Cascade

- Example: 4 stage frequency divider

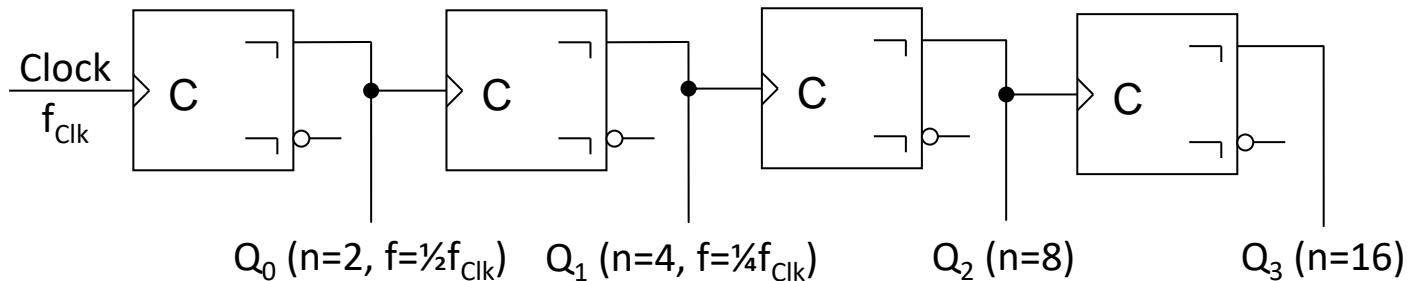

Prescalers (4)

- 4024 – 7-stage frequency divider

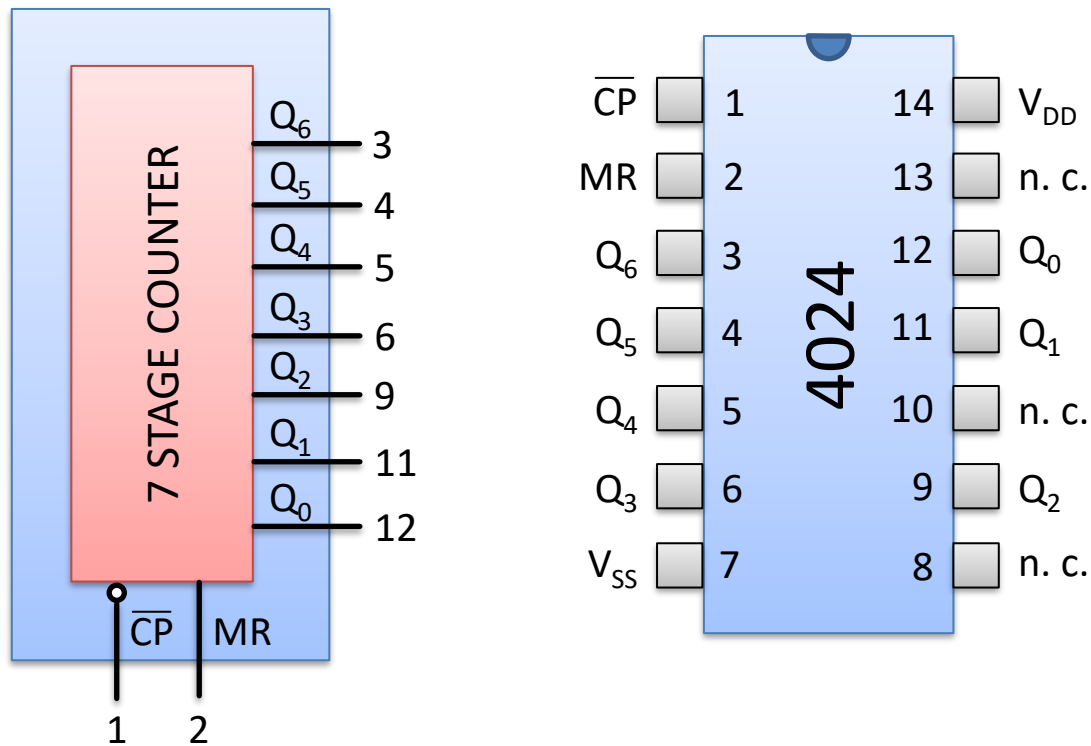

Prescalers (5)

- 4024 – 7-stage frequency divider (continued)

| Symbol | Pin | Description |
|-------------------------------------|-----------------------|---------------------------|
| \overline{CP} | 1 | clock input |
| MR | 2 | master reset input |
| V_{SS} | 7 | ground |
| n. c. | 8, 10, 13 | not connected |
| $Q_0, Q_1, Q_2, Q_3, Q_4, Q_5, Q_6$ | 12, 11, 9, 6, 5, 4, 3 | buffered parallel outputs |
| V_{DD} | 14 | supply voltage |